Total N	No. of Questions : 8] SEAT No.	:	
<b>PB45</b>	531 Y	[Total No. of Pages :3	
	[6261]-44 S.E.(Computer Engineering)		
	DIGITAL ELECTRONICS AND LOGIC DESI	IGN	
	(2019 Pattern) (Semester - III) (210245)	IGIV	
	2½ Hours]  ctions to the candidates:	[Max. Marks:70	
1 <i>nstruc</i> 1)			
2)			
3)	Assume Suitable data if necessary.		
<b>Q1)</b> a)	) What are the applications of Flip-Flop? Explain shift reg	gister. [6]	
b`	) Design a sequence generator to generate the sequence.	[6]	
,			
<b>c</b> )	Desgin the 2-bit synchronous UP counter using T - F/F.	[6]	
	OR O		
<b><i>02</i></b> ) a)	) Explain S-R Flip-Flop and J-K Flip Flop using NOR ga	te. [6]	
<b>L</b> - <b>/</b> ··)		[0]	
b`	) Convert the following Flip Flops	.[6]	
,	i) D to T		
	ii) Jk to D		
<b>c</b> )	) Draw and explain 4 bit Ripple down Counter.	(6)	
		\$.	
(12) ~)	Convert the following Flip Flops i) D to T ii) Jk to D  Draw and explain 4 bit Ripple down Counter.  Implement the following Boolem function using PAL. $F1 = \sum m(0,3,5,7,9,10,11,14,15)$ $F2 = \sum m(2,3,12,14)$		
<b>Q3)</b> a)	Implement the following Boolem function using PAL. $ \Sigma_{\text{max}}(0.2.5.7.0.10.11.14.15) $	[0]	
	$\Gamma 1 = \angle M(0,3,3,7,9,10,11,14,13)$		
	$F2 = \sum m(2,3,12,14)$		

Draw block diagram of PLA device and explain in detail. b) [6]

What is ASM chart? Design ASM chart for 3-Bit gray code sequence with up-down conditions.

OR

P.T.O. c) [5]

Q4)	a)	Implement gray to binary code using PLA.	[6]
	b)	Implement the following Boolean functions using PAL	[6]
		$X1(A, B, C, D) = \sum m(0, 2, 6, 7, 8, 9, 12, 13)$	
		$X2(A, B, C, D) = \sum m(3, 6, 7, 11, 14, 15)$	
	c)	What is ASM Chart? State & Explain basic components of ASM ch	art.
		Also explain the salient features of ASM chart	[5]
		(C) 1/6,	
<b>Q5</b> )	a)	Draw and explain the operation of TTL NAND gate using 2-bit input	t.
			[6]
	b)	Explain with a neat diagram CMOS NAND gate	[6]
	c) (	Define the following terms and mention its standard value for TTL	
		logic family.	[6]
		i) Noise immunity	. ,
		ii) Power Dissipation	
		iii) Figure of Merit	
		OR	
06)	a)	Draw and explain CMOS invertor.	163
20)	uj	Diaw and explain excess in error.	
	b)	Explain TTL open collector.	[6]
		20.	[6]
	c)	Compare CMOS and TTL logic family.	[6]
<b>Q</b> 7)	a)	For memory operations draw digital circuits using ALU and shift regis	tes.
~ /	,		[6]
	b)	What is Microprocessor? List different applications of Microprocess	
			[6]
	c)	What are the different types of buses used in Microprocessor?	[5]
	,	Jr == == = == == == == == == == == == ==	(* J
		OR OR	
[626	51]-4	2	

Q8)	a)	Explain in brief basic arithmetic operations using ALU IC 74181.	[6]
	b)	Write a short note on i) Address Bus ii) Data Bus iii) Control Bus	[6]
	c)	Write a short note on Memory organization of Microprocessor.	[5]
		A 3 Kenter of the state of the	86. J.
		CE 30 1 105 105 105 105 105 105 105 105 105	
[626	1]-4	3 👸	